



Investigations on Stacked Multilevel Inverter Topologies for Induction Motor Drives

Viju Nair. R


Research Supervisor: Prof. K . Gopakumar
Department of Electronic Systems Engineering
Indian Institute of Science
Bangalore, India.

Overview of presentation



- Adjustable speed AC drive systems
- Multilevel inverters and their features
- Motivation for stacked multilevel inverters
- Nine level stacked inverter for 3-phase IM drives
- Conclusion and future scope

Adjustable speed AC drive system

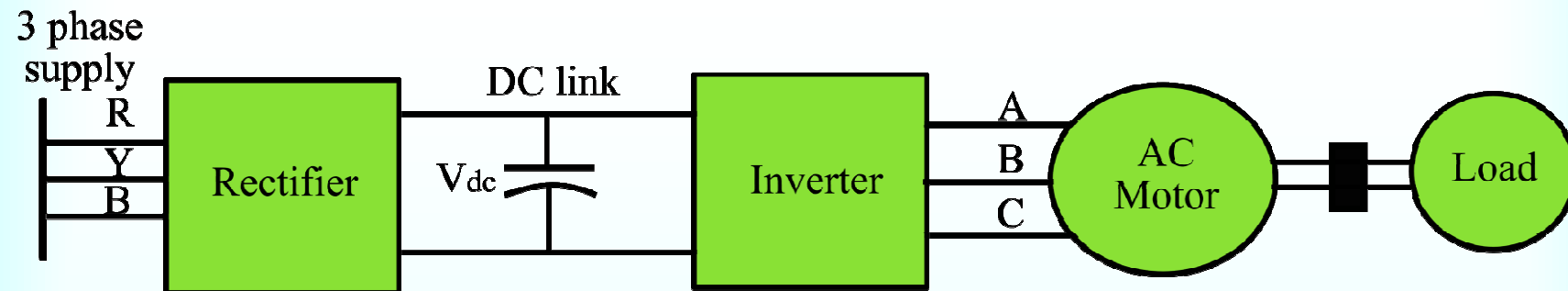



Important modules of an adjustable speed AC drive system are,

- Rectifier
- Three phase Inverter
- AC motor


3 phase conventional two level Inverter



3 phase 2 level inverter

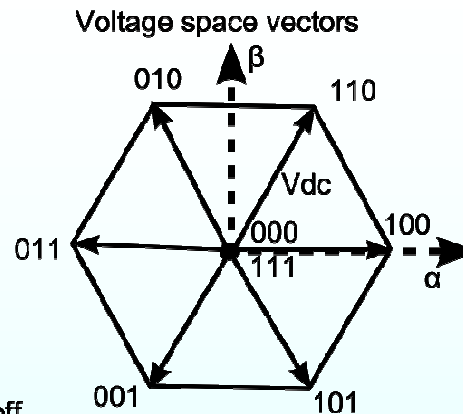 

Inverter waveforms

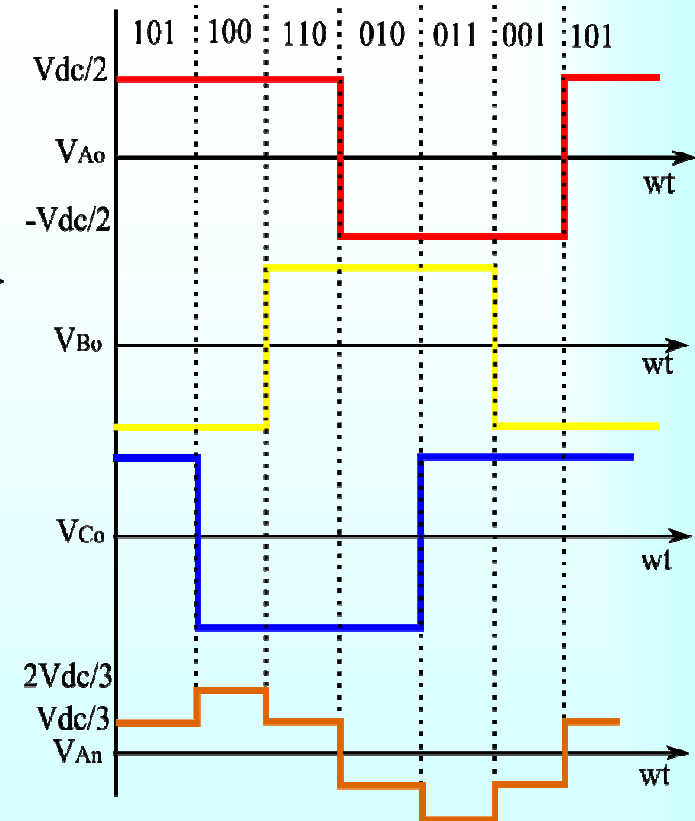

- 8 (2^3) switching states possible
- Only 2 voltage levels in the pole voltage waveforms
Hence called as two level inverter

- V_{Ao} is defined as inverter pole voltage.
- V_{An} is defined as motor phase voltage.

Multilevel inverters and their features



Multilevel inverters have more number of levels in the pole voltages and therefore have the following additional features

- Improved voltage and current THD
- Reduced switching frequency
- Reduced EMI issues
- Reduced filtering requirements


Commonly used multilevel inverter topologies are

- Diode clamped inverter
- Flying capacitor inverter (FC)
- Cascaded H-bridge inverter (CHB)
- Hybrid multilevel inverter

Multilevel inverter topologies




5 level diode clamped inverter

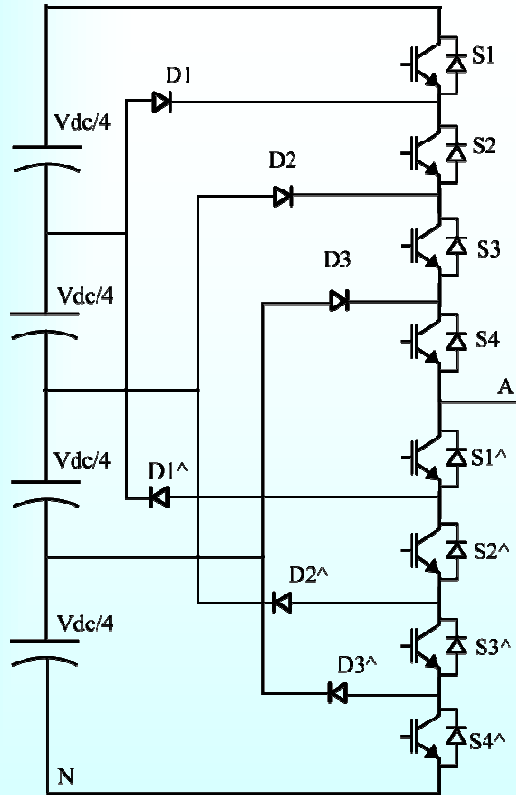


- Requires clamping diodes
- DC link capacitor voltage balancing is difficult

5 level flying capacitor inverter

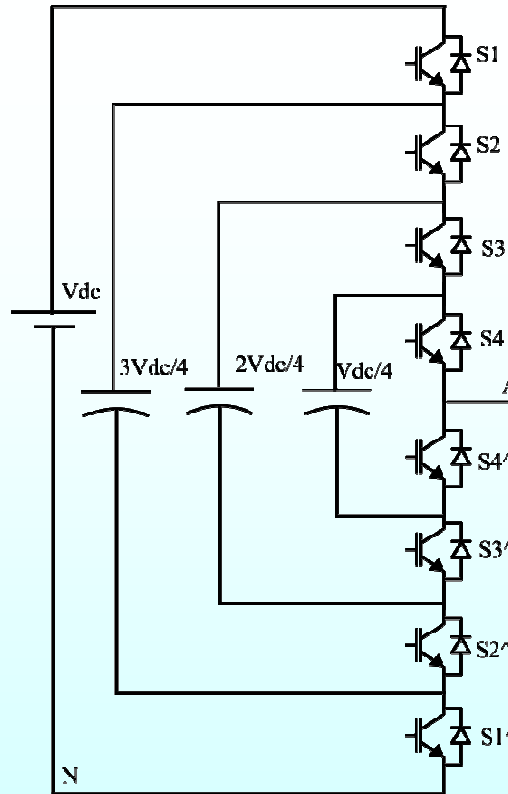

- As the number of voltage levels increases capacitor voltage balancing is difficult

5 level cascaded H-bridge inverter

 


- Modular structure
- Requires multiple DC supply for operation

Multilevel inverters.....continued




- Hybrid multilevel inverters by combining FC and CHBs

- 5-level Inverter [1] :

 

Generates pole voltages: $0, V_{dc}/4, 2V_{dc}/4, 3V_{dc}/4, V_{dc}$ (V_{AN})

- 17-level Inverter [2]:

 

Generates pole voltages: $0, V_{dc}/16, 2V_{dc}/16, 3V_{dc}/16, \dots, V_{dc}$ (V_{AN})

[1] P. Roshan kumar, P. Rajeevan, K. Mathew, K. Gopakumar, J. Leon, and L. Franquelo, "A five-level inverter topology with single-dc supply by cascading a flying capacitor inverter and an h-bridge," IEEE Trans. Power Electron., vol. 27, no. 8, pp. 3505–3512, Aug 2012.

[2] P. Roshan Kumar, S. Kaarthik, K. Gopakumar, J. Leon, and L. Franquelo, "Seventeen-level inverter formed by cascading flying capacitor and floating capacitor h-bridges," IEEE Trans. Power Electron., vol. 30, no. 7, pp. 3471–3478, July 2015.

Motivation for stacked inverters




- Basic Inverter topologies when extended to higher levels face difficulties in capacitor balancing like in diode clamped and flying capacitor inverters
- Also their device count drastically increases on increasing the number of levels
- Cascaded H-bridge inverters needs multiple isolated DC sources which limits its applications
- Hybrid inverters formed by combination of FC and CHB cannot be scaled for obtaining higher number of levels since the capacitor voltages match with the switch voltage drops

**A new method for generating higher number of levels in the voltage waveform -
Stacked Multilevel Inverters**



Generation of Higher number of Voltage Levels by Stacking Inverters of Lower Multilevel Structures with Low Voltage Devices for Drives

Nine level stacked inverter

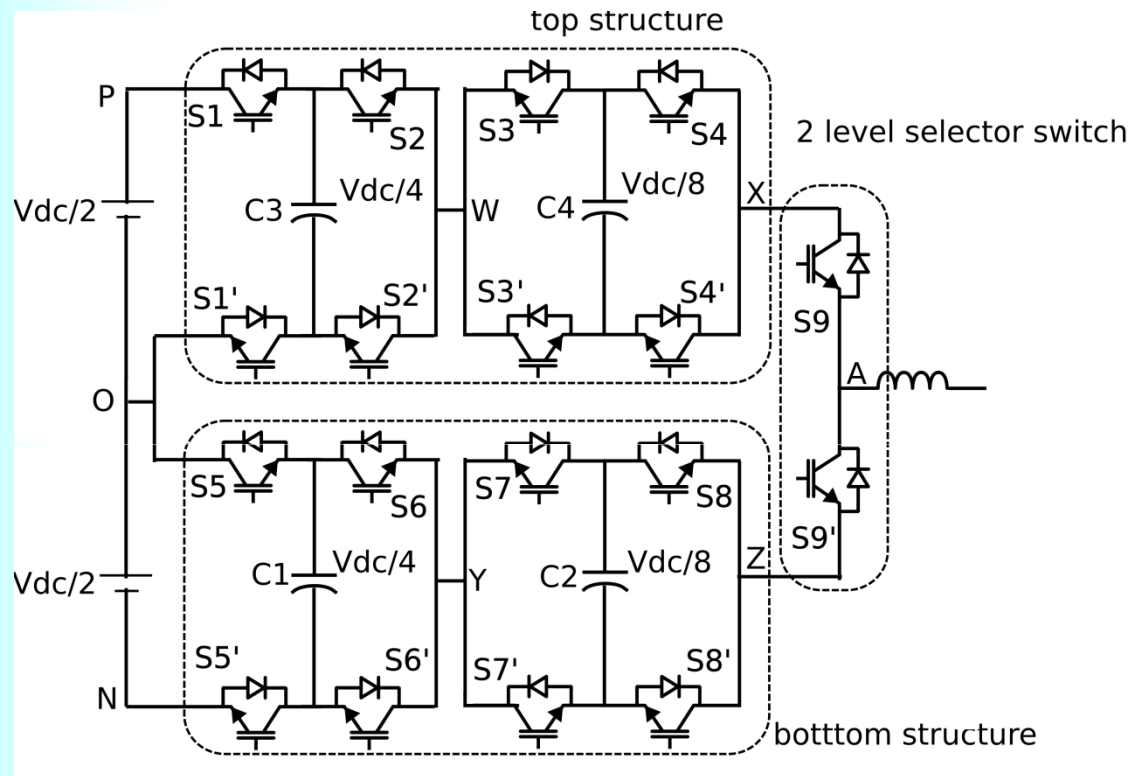

Power circuit schematic for the stacked 9-level inverter by stacking two 5-level inverters for phase 'A'


Note: S1-S1', S2-S2'S9-S9' are complimentary switches

- Bottom structure generates pole voltages (V_{ZN}): 0, $V_{dc}/8$, $V_{dc}/4$, $3V_{dc}/8$, $V_{dc}/2$ with respect to 'N'
- Top structure generates same pole voltages with respect to 'O' (V_{XO})
- With respect to 'N', top structure generates $V_{dc}/2$, $5V_{dc}/8$, $3V_{dc}/4$, $7V_{dc}/8$, V_{dc} (V_{XN})
- Thus stacked inverter generates the nine pole voltages (V_{AN})
- 2-level selector switch connects the respective outputs to the machine terminals

Stacked inverter.....continued



- Top structure modulates the section-1 and bottom structure modulates the section-2 to generate the respective pole voltages
- So the selector switches need to switch only at fundamental frequency
- In each carrier region, the carrier and modulating signal are compared and the pole voltage switch between the 2 levels
- Above pole voltages will be generated only if the capacitor voltages are maintained at their respective values
- This is achieved using the switching state redundancies available with each of the pole voltages

 

Carrier based PWM

Stacked inverter - capacitor voltage control example




The 3 figures shows the multiple ways to achieve a pole voltage of $5V_{dc}/8$

Fig	Switching state	C3	C4
a	0001	Unaffected	Discharging
b	0110	Discharging	Charging
c	1010	Charging	Charging

- The table is for positive direction of current
- A tolerance band is defined for each of the capacitor voltage references
- Appropriate switching state is selected to maintain the voltages
- Switching state redundancies exist for all the pole voltages

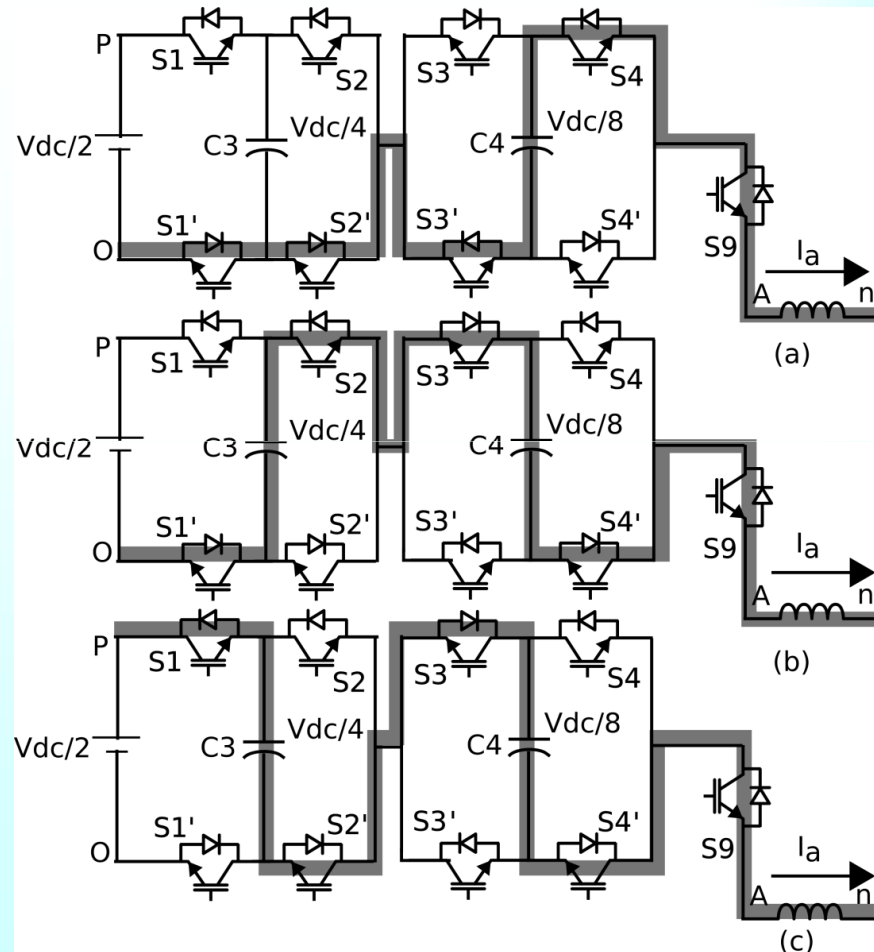Note: '1' indicates top switch is ON. '0' indicates bottom switch is ON



Capacitor voltage control.....continued




- So a switching state is finally decided by the pole voltage, capacitor voltage status (H_{ax} , $x=1,2,3,4$) and the current direction as shown in the table

Ia	Ha1/Ha3	Ha2/Ha4	Switching State Selected (S1,S2,S3...S9)		
			Vdc/8	Vdc/4	3Vdc/8
+	0	0	000010100	000010110	000011100
+	0	1	000000010	000010110	000010010
+	1	0	000001100	000001110	000011100
+	1	1	000000010	000001110	000001010
-	0	0	000000010	000001110	000001010
-	0	1	000001100	000001110	000011100
-	1	0	000000010	000010110	000010010
-	1	1	000000010	000010110	000011100

“+” indicates current flowing out from pole “A” . Switch state “1” indicates switch is ON.
 $H_{ax}=1$ implies capacitor needs discharging to maintain voltages with in tolerance band

- All the capacitor voltages and current directions are sensed in DSP and send to FPGA in every switching cycle along with pole voltage and PWM timing
- Above table is stored in FPGA which selects the correct switching state based on the inputs from DSP

Implementation block diagram

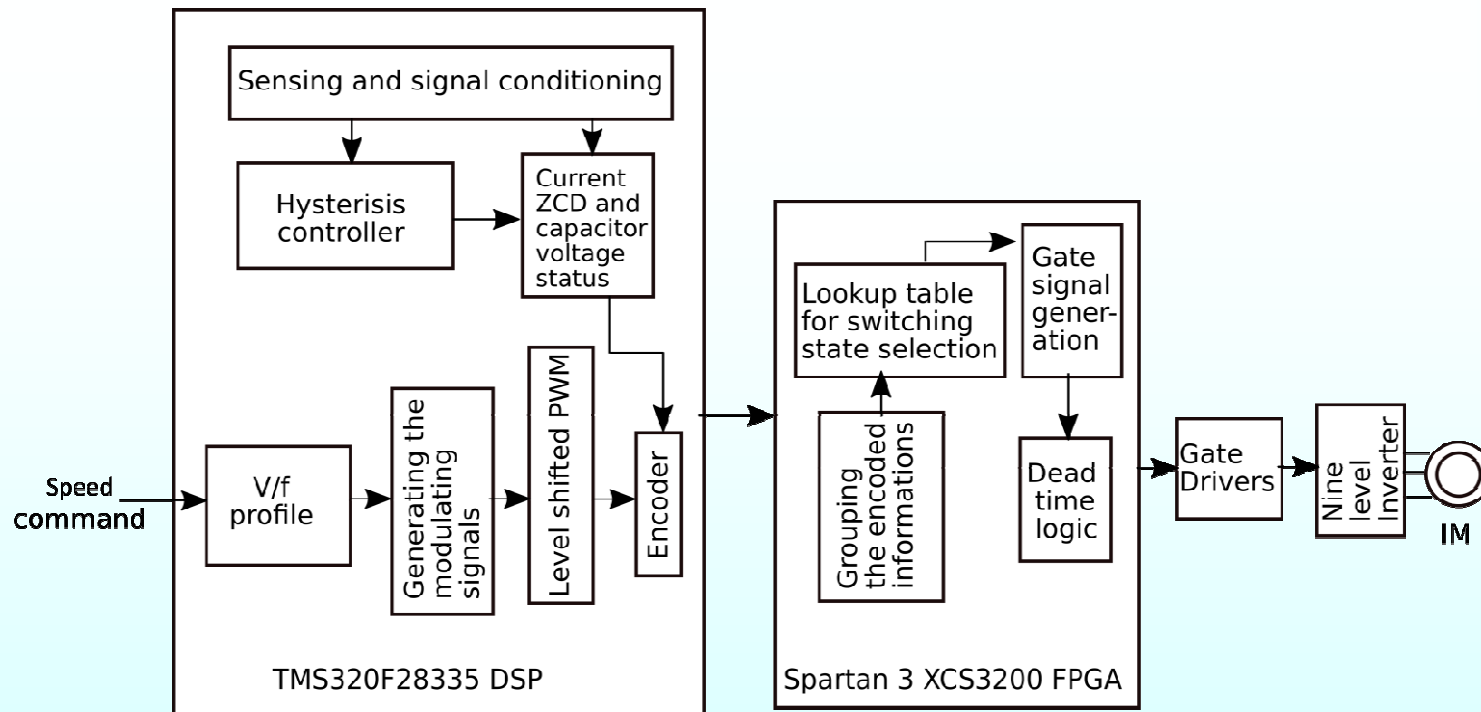

- Switching frequency = 2kHz
- 3-phase, 415V, 7.5kW, 50Hz IM is used
- All the capacitors are 2200uF

Capacitor sizing



- The capacitor sizing is done by using the relation,

$$C = \frac{I_p}{f_s * \Delta V}$$

where,


I_p = peak capacitor current (10A)

f_s = minimum sampling frequency (1800Hz)

ΔV = peak to peak capacitor voltage ripple (2.5V)

- So for conducting the experiment, the capacitance value is selected as 2200 μ F for all the three phases


Experimental results

 


(a) Modulating signal and generated pole voltages
x-axis: 10ms/div

- 1) Inverter pole voltage (V_{AO}): 100V/div
- 2) Modulating signal
- 3) Gate signal to selector switch
- 4) Positive half of modulating signal
- 5) Top structure pole voltage (V_{XO}): 20V/div
- 6) Negative half of modulating signal
- 7) Bottom structure pole voltage (V_{ZO}): 100V/div

Experimental results at steady state

 


(b) 10Hz , x-axis: 20ms/div

 


(c) 20Hz , x-axis: 10ms/div

- 1) Motor phase voltage (V_{An}) : 100V/div
- 2) Inverter pole voltage (V_{AO}): 100V/div
- 3) Capacitor voltage ripple (V_{c3}): 5V/div
- 4) Phase current (I_a): 2A/div.

Steady state resultscontinued

 


(d) 30Hz , x-axis: 10ms/div

 

(e) 45Hz , x-axis: 5ms/div


- 1) Motor phase voltage (V_{An}) : 100V/div
- 2) Inverter pole voltage V_{AO}): 100V/div
- 3) Capacitor voltage ripple (V_{c3}): 5V/div
- 4) Phase current (I_a): 2A/div.

Transient results

 

(f) Motor acceleration, x-axis: 500ms/div

 
- 1) Motor phase voltage (V_{An}): 50V/div
- 2) Capacitor voltage ripple (V_{c4}): 5V/div
- 3) Capacitor voltage ripple (V_{c3}): 5V/div
- 4) Phase current (I_a): 5A/div.



(g) Motor starting, x-axis: 1s/div


- 1) Motor phase voltage (V_{An}): 50V/div
- 2) Capacitor voltage (V_{c4}): 20V/div
- 3) Capacitor voltage (V_{c3}): 20V/div
- 4) Phase current (I_a): 10A/div.

Experimental results.....continued

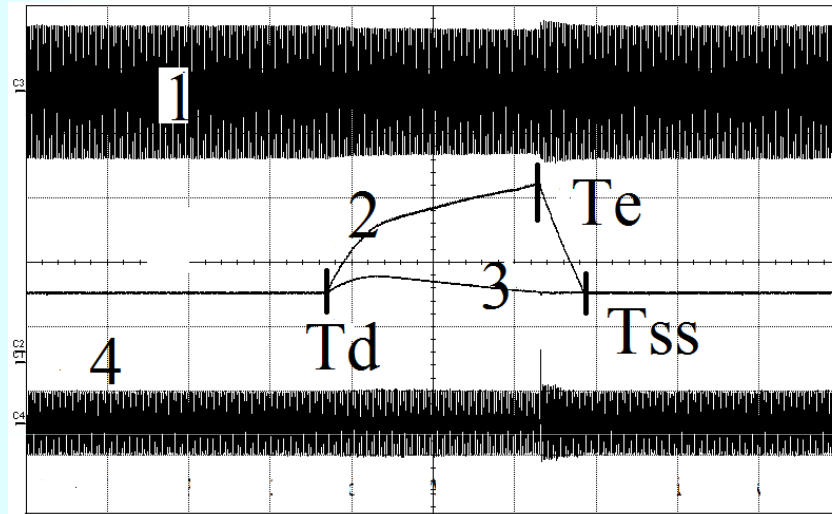

(h) Capacitor balancing test, x-axis: 10ms/div

 
- 1) Motor phase voltage (V_{An}): 50V/div
- 2) Capacitor voltage (V_{c4}): 20V/div
- 3) Capacitor voltage (V_{c3}): 50V/div
- 4) Phase current (I_a): 2A/div.



(i) FC and H-bridge switching, x-axis: 5ms/div

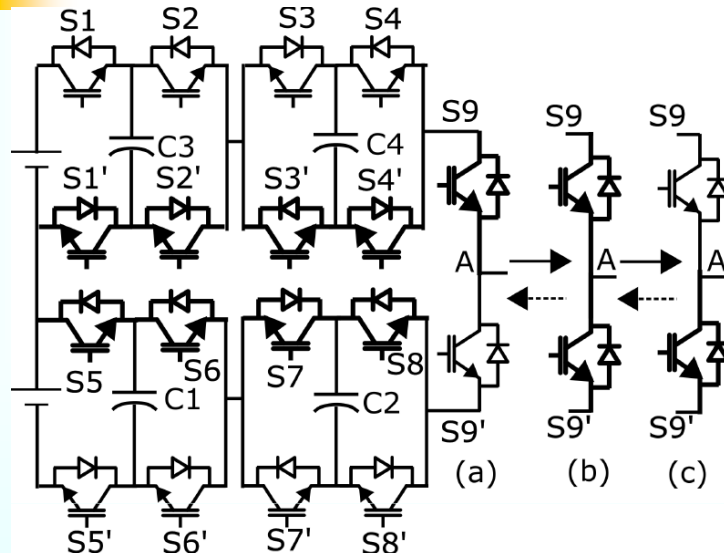- 1) Modulating signal
- 2) Top FC pole voltage: 100V/div
- 3) Bottom FC pole voltage: 100V/div
- 4) Top H-bridge switching : 20V/div
- 5) Bottom H-bridge switching: 50V/div


Soft cycle commutation for selector switches



In figure, darkened switches are ON

- When the bottom structure is operating, switches, S1', S2', S3', S4' are kept ON
 - When the top structure is operating, switches S5, S6, S7, S8 are kept ON
 - It is done to reduce the voltage rating of selector switches to $V_{dc}/2$
- When transiting from positive half to negative half cycle, if S9' is turned ON before S9 turns off, then S9 can undergo a zero voltage switching OFF and S9' can undergo a zero voltage switching ON (solid arrow in fig)
 - Zero voltage switching can be done during the reverse transition also (dotted arrow)
 - It helps to minimize the switching losses in the selector switches

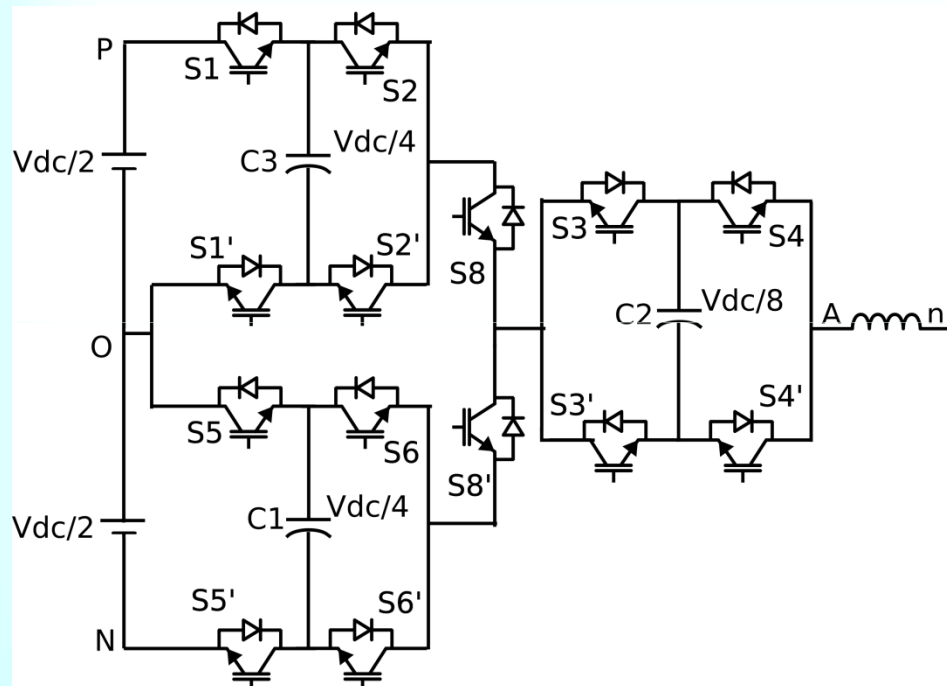Reduced device count power circuit for stacked inverter [1]



- The H-bridges can be made common by connecting the selector switches in between
- Here the number of switches and capacitors are reduced but now the H-bridges have to switch throughout the cycle
- The FC switches still need to operate only in one half of fundamental cycle
- If the H-bridges fails, inverter can still operate as 5-level inverter in the entire modulation range with rated power

[1] Viju Nair R, Arun Rahul S, Sudarshan Karthick, Abhijit Kshirsagar, K Gopakumar, "Generation of Higher Number of Voltage Levels by Stacking Inverters of Lower Multilevel Structures with Low Voltage Devices for Drives", accepted in IEEE Transactions on Power Electronics

Conclusion



- Stacked inverter generates higher number of voltage levels with inherent capacitor balancing capabilities
- All the capacitors can be balanced irrespective of any modulation index and load power factor
- Stacking reduces the DC supply requirement at front end
- The switching loss associated with the selector switches are minimised through soft cycle commutation (switching at fundamental frequency only)
- The FC and H-bridge switches used are of low voltage ratings ($V_{dc}/4$, $V_{dc}/8$)
- The FC switches need to operate only in one half of fundamental cycle
- The inverter can operate in lower number of voltage levels in case of failure of H-bridge for the rated power in entire modulation range
- This method of stacking can be extended to obtain still higher number of voltage levels and the inverter can be driven directly from low voltage battery cells (EV)